-						_
	National					
	Qualificati	ONS		DCT	Mar	k
	ZUZI ASSE	SSIVIEINI r	KESUU	KCE		
X823/76/01			E	Engine	ering S	Science
Duration — 2 hours 30 min	nutes			*	X 8 2 3	7601*
Fill in these boxes and rea	d what is printed	below.				
Full name of centre			Town			
Foronomo(s)	Curo	200			Numbo	r of cost
	Sum	ame				i oi seat
Date of birth						
Day Month	Year	Scottish ca	ndidate r	number		
Total marks — 110			I			
SECTION 1 — 20 marks						
Attempt ALL questions.						
SECTION 2 — 90 marks Attempt ALL questions.						
Show all working and unit	s where appropri	iate.				
You should refer to the Hig The number of significant	gher Engineering figures expressed	Science Data 1 in a final an	Booklet v swer shoi	which you uld be eau	have been ivalent to	given. the least
significant data value give	n in the question	. Answers that	t have tw	o more fig	gures or on	e less
Write your answers clearly	in the spaces pro	ovided in this	booklet.	Additiona	l space for	answers is
provided at the end of this number you are attemptin	s booklet. If you ι g.	ise this space	you mus	t clearly ic	lentify the	question
Use blue or black ink.	•					/
		الفاعينين طمري	ب ب ا ا م م	a + h -		
Invigilator; if you do not, y	ation room you n ou may lose all tl	nust give this ne marks for t	booklet t his pape:	o the r.	×	SQA
Invigilator; if you do not, y	ation room you n ou may lose all ti	nust give this ne marks for t	booklet t his pape	o the r.	×	ŚQĄ

.my/ tps





MARKS DO NOT WRITE IN THIS MARGIN

3

2. An op-amp circuit is shown below.



Calculate V_{OUT} .



[Turn over



MARKS DO NOT WRITE IN THIS MARGIN A walkway has a uniformly distributed load and point load applied as shown 3. in the diagram below. 6•3 kN - 0∙75 kN m⁻¹ 65° В 4∙2 m 1.5 m Calculate the magnitude and direction of the reaction force at B. 5



١.	The ship shown below is used to transport liquefied natural gas.	MARKS	DO NOT WRITE IN THIS MARGIN
	Describe two pieces of specialised knowledge required by a structural engineer during the design of the ship.	2	
	Knowledge 1	-	
		-	
	Knowledge 2	-	
		-	
		-	
	[Turn over		

L



5. A motor is used in the cooling system within a mini fridge.



MARKS DO NOT WRITE IN THIS MARGIN

1

(a) The motor has a power rating of 4.6 W and 12 V. Calculate the resistance of the motor.





6. A logic diagram is shown below.



Draw a NAND equivalent for this circuit. Simplify if appropriate.

4

MARKS DO NOT WRITE IN THIS MARGIN



[Turn over for next question

DO NOT WRITE ON THIS PAGE



DO NOT WRITE IN

THIS

7. An engineering team produced a prototype system to smooth sand in a long jump pit once an athlete has completed their jump.



The system must meet the following specification.

- i. An operator presses a switch to begin the smoothing process
- ii. The rake moves forward at full speed until limit switch 1 is pressed
- iii. The rake then moves backward at half speed until limit switch 2 is pressed
- iv. If an overhead sensor indicates that the pit is not fully smooth then an agitator motor switches on and steps ii and iii are repeated once
- v. The system resets and waits for the next press of the operator's switch

Input	Pin	Output
	7	rake motor forward
	6	rake motor backward
	5	agitator motor
overhead sensor (high — when smooth surface sensed)	3	
limit switch 2	2	
limit switch 1	1	
operator switch	0	



7. (continued) MARKS DO NOT WRITE IN THIS MARGIN (a) Draw a flowchart to show the control of the smoothing system. 8



MARKS DO NOT WRITE IN THIS MARGIN

7. (continued)

An alternative method of controlling the rake motor is shown below. When current flows from left to right through the motor it will spin clockwise.



(b) Describe, with reference to the output pins shown above, how the motor could be made to rotate in each direction and switch off.





8. Plants need to be kept in a polytunnel with a constant light level to ensure they grow correctly. This is done by using banks of powerful LEDs to provide additional light when the outside light level drops.

The initial design for the electronic control system is shown below. The light sensor monitors the light level **outside** the polytunnel.



(a) Describe, with reference to this circuit, the operation of the LED connected to op-amp 1 as the outside light level decreases from a high level to a low level.

3

MARKS DO NOT

THIS



During testing, it was found that the system did not work as well as expected, so it was redesigned. A diagram of the redesigned circuit is shown below.

DO NOT WRITE IN THIS MARGIN

In this instance, the light sensor was placed inside the polytunnel.





The LEDs are at their most efficient when a current of $5 \cdot 2$ mA flows through each one. They are also found to have a $2 \cdot 3$ V drop across them when they are on.

(e) Calculate the required resistance for the protective resistors to ensure maximum efficiency.

 $+V_{cc}$ for the comparators is set to 8.0 V. The comparator saturates at 85%.

MARKS DO NOT WRITE IN THIS MARGIN

3

A further solution involving the use of a microcontroller is also tested, and is shown below. One output pin on the microcontroller activates a bank of LEDs.



By using pulse width modulation, the LEDs can be made to appear bright or dim.

Code for the test is shown below, in **PBASIC** and **Arduino**.

main:	int Sensor = A0;
readadc pin0, b0	int LEDBank = 7;
if b0 <50 then level1	<pre>void setup() {</pre>
if b0 <100 then level2	pinMode(LEDBank, OUTPUT);
if b0 <150 then level3	}
let mark = 0	<pre>void loop() {</pre>
let space = 10	int reading=analogRead(Sensor);
goto pulser	int value=map(reading,0,1023,0,255); if(value<50) {
level1:	digitalWrite(LEDBank, HIGH);
let mark = 10	delay(10);
let space = 0	digitalWrite(LEDBank, LOW);
goto pulser	delay(0);
	}
level2:	if(value>49&&value<100) {
let mark = 6	digitalWrite(LEDBank, HIGH);
let space = 4	delay (6);
goto pulser	digitalWrite(LEDBank, LOW);
	delay (4);
level3:	}
let mark = 3	if(value>99&&value<150) {
let space = 7	digitalWrite(LEDBank, HIGH); delay(3);
pulser:	digitalWrite(LEDBank, LOW);
high 7	delay(7);
pause mark	}
low 7	else {
pause space	digitalWrite (LEDBank, HIGH);
	delay (0);
goto main	digitalWrite (LEDBank, LOW);
	delay (10);
	}
	}



DO NOT WRITE IN THIS MARGIN [BLANK PAGE]

Г

L

DO NOT WRITE ON THIS PAGE



(f) Explain, with reference to the code and the circuit, the effect on the	4
	LED'S when the reading from the analogue sensor rises from 5 to 200.	4
		_
		_
		_
		_
		_
		_
		_
Т	he logic circuit shown below controls a valve that provides water for the	
F	lants.	
(g) Complete a Boolean equation to describe the operation of this circuit.	4
	Z =	_

9. A pneumatic circuit is needed to feed waste into an incinerator as part of a system to produce electricity from rubbish. For safety reasons, a barrier must be raised before material is pushed in.

DO NOT WRITE IN THIS MARGIN

The system must also allow both cylinders to be outstroked to allow for maintenance, and must have an emergency feature to immediately close the barrier and withdraw the ram if required.



The pneumatic circuit is triggered by the electronic circuit shown below. The relay requires 56 mA (I_c) to activate.





o (MARKS	DO NO VRITE THIS MARG
9. (c (a	Calculate the minimum base current (I _b) required to switch on the relay.	1	
(b	Calculate the voltage required across the variable resistor.	2	
	(Assume V _{be} is 0·7 V)	7	
(c)	Calculate the current through the variable resistor.	1	
		_	
	[Turn ove	r	

At a later point in the testing process I_b was found to be 1.35 mA, and the current through the variable resistor was 1.09 mA. The variable resistor was still set at 2.5 k Ω .



(d) Calculate the resistance of the type 6 thermistor and, using the graph above, find the temperature of the thermistor.

5



MARKS DO NOT WRITE IN THIS MARGIN



- (e) Describe, with reference to the circuit shown above, what happens when valve (A) is actuated by the relay.
- 6



MARKS DO NOT WRITE IN THIS MARGIN

2

9. (continued)

(f) Explain, giving two reasons, why using a microcontroller based system with solenoid actuated 5/2 valves controlling the cylinders would be a preferred solution.



[Turn over for next question

DO NOT WRITE ON THIS PAGE



10. An engineering company has designed a railway tunnel for a new rail line through a major city.

A boring machine is used to excavate the tunnel.



- (a) Civil and environmental engineers play a critical role in all phases of the project.
 - (i) Describe two roles of a civil engineer during the planning phase of the project.

2

MARKS DO NOT WRITE IN THIS MARGIN





MARKS DO NOT WRITE IN THIS MARGIN (continued) 10. (b) A second machine with a diameter of 12.4 m follows the boring machine to smooth the surfaces of the tunnel. Three cutting blades, rotating at 9.93 revs min⁻¹, are powered by a motor. Each cutting blade exerts a force of 924 N on the rock surface. Ø12·4 m cutting blade (i) Calculate the total torque produced by the motor. 2 2 (ii) Calculate the output power of the motor.





The boring machine, with mass 120,000 kg is lowered to a depth of 42.6 m.

MARKS DO NOT WRITE IN THIS MARGIN

3

The brakes used to control the rate of descent have a mass of 88 kg and a specific heat capacity of 910 $Jkg^{-1}K^{-1}$. The brake temperature at the start of the operation is 17 °C.

(d) Calculate the final brake temperature.

The final design of the structure used to support the weight of the boring machine during the lowering process is shown below.





(e) Complete, using nodal analysis, the table of the missing forces and their natures.

MARKS	DO NOT WRITE IN THIS MARGIN

6

Member	AB	AC	BC	BD	CD	CE
Force			583 kN	566 kN		
Nature	tie	strut	strut	tie		

Space for calculations		



11. The V&A museum is part of the new waterfront project in Dundee. As part of the project, teams of engineers have been working on improvements to Dundee railway station and the road network in the city centre.
Image: Comparison of the city centre is the city centre is

(a) Explain, with reference to two social impacts, why cities make improvements to railway stations and road networks.

Impact 1 _____ Impact 2 _____

4



(b) In the museum, a new exhibit is suspended from the ceiling using cables as shown below.



The force W represents the weight of the exhibit and is acting 1.4 m from point B. The distance from A to B is 3.46 m.

(i) Draw a free body diagram of the forces acting on the exhibit.

2

2

(ii) Calculate the force, W.



MARKS DO NOT WRITE IN THIS MARGIN





(d) A replacement exhibit is to be suspended from the ceiling in the same position.

The two cables supporting the new exhibit hanging from the connecting ring are replaced with a hollow aluminium alloy tube.



The 2.7 m long tube has a diameter of 72 mm and a wall thickness of 2.5 mm. It supports a load of 32.7 kN.

(i) Calculate the change in length of the tube when it is loaded with the new exhibit.

6

MARKS DO NOT WRITE IN THIS MARGIN





[END OF QUESTION PAPER]



MARKS DO NOT WRITE IN THIS MARGIN

ADDITIONAL SPACE FOR ANSWERS



ADDITIONAL SPACE FOR ANSWERS



[BLANK PAGE]

DO NOT WRITE ON THIS PAGE



[BLANK PAGE]

DO NOT WRITE ON THIS PAGE

Acknowledgement of copyright

- Question 4Gas tanker: Oleksandr Kalinichenko/shutterstock.comQuestion 5Mini fridge: AnEduard/shutterstock.com
- Question 10 Tunnel machine: PI/shutterstock.com
- Question 11 V&A Dundee: Joe Dailly/shutterstock.com

