	FOR OFFICIAL USE					
E.	National Qualificatio	ons				Mark
	2024				Г	
X823/76/01				Engin	eering	g Science
FRIDAY, 17 MAY				I		
9:00 AM - 11:30 AM					* X 8 2	37601*
Fill in these boxes and rea	ad what is printed	below.	Town			
Forename(s)	Surna	me			Num	ber of seat
Date of birth Day Month	Year	Scottish ca	ndidat	e number		
Total marks — 110 SECTION 1 — 20 marks Attempt ALL questions. SECTION 2 — 90 marks Attempt ALL questions.						
Show all working and unit You should refer to the His The number of significant significant data value give figure than this will be acc Write your answers clearly provided at the end of thi number you are attemptin Use blue or black ink.	gher Engineering So figures expressed in in the question. A cepted. v in the spaces prov s booklet. If you us g.	cience Data in a final an Answers tha rided in this e this space	swer sh t have bookle you m	nould be ec two more f et. Addition ust clearly	quivalent igures or al space	to the least one less for answers is
Before leaving the examin Invigilator; if you do not, y	•	-			\rightarrow	XSQA
_	* X 8 2 3	3 7 6 0 1	₩₩₩₩ ^{0 1} *ſ	Downloade	d free fr	© om https://sq

ſ

a.my/

SECTION 1 — 20 marks Attempt ALL questions


1. A control circuit is required for a home security system.



As part of the design for the home security system, an electronic engineer needs a digital logic circuit to satisfy the Boolean equation, shown below.

$$\mathsf{Z} = \left(\overline{\mathsf{A} \cdot \mathsf{B}}\right) \cdot \left(\mathsf{C} + \mathsf{D}\right)$$

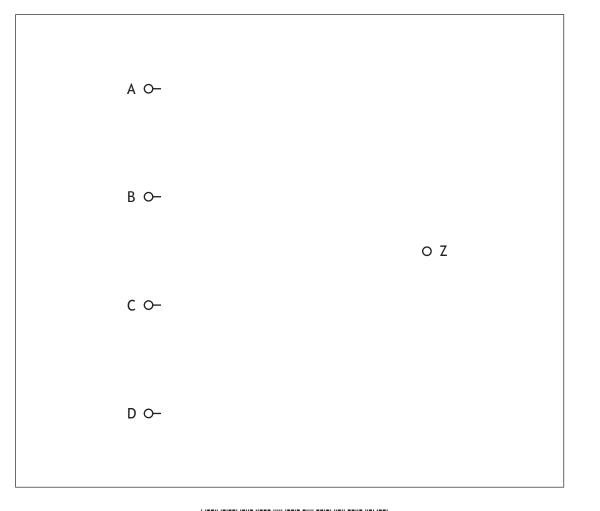Draw a digital logic circuit for this Boolean equation.





MARKS DO NOT WRITE IN THIS MARGIN

2. A coastguard rescue helicopter is used to lift a stranded casualty from the sea.




A motorised lifting mechanism has a drum diameter of 0.84 m.

The mechanism lifts a coastguard, the casualty and a stretcher of mass 76 kg, 95 kg and 18 kg respectively.

Calculate the torque acting on the drum.



3. A beam is being tested.

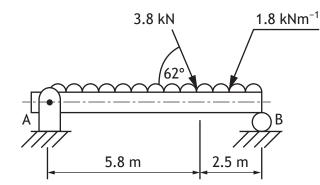

The beam is subjected to loading as shown above.


Calculate, by taking moments about A, the vertical reaction at B.



MARKS DO NOT WRITE IN THIS MARGIN 4. A range of electronic circuits are used to control a night-time water fountain show. The water fountain show is made from a number of individual water jets. The following circuit is part of the system used to operate one of the water jets. 54 kΩ 18 kΩ 5.0 V O- $+V_{CC}$ 36 kΩ 5.0 V O-18 kΩ $-V_{\rm CC}$ 5.0 V O- $\mathsf{V}_{\mathsf{out}}$ 0 V O-Calculate the output voltage ($\mathrm{V}_{\mathrm{out}}$) from the operational amplifier (op-amp) shown 2 above.



page 05

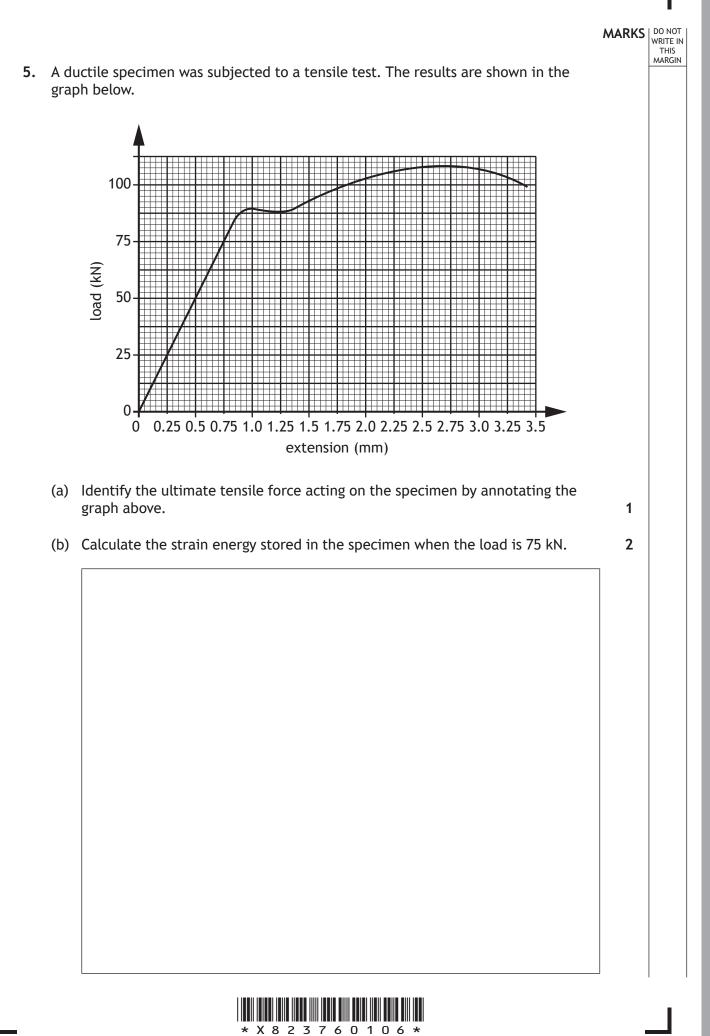

page 06

			MARKS	DO NOT WRITE IN THIS MARGIN
5.	(cor	ntinued)		
	(c)	Describe the effect on the specimen shown opposite, when a force of 50 kN is applied and then removed.	1	
			_	
			_	
			-	
	(d)	Sketch, on the same axes on the graph opposite, a load-extension graph of a more brittle material than the original specimen tested.	1	
		[Turn over	r	



6. An electronic engineer has written code to control a microcontroller-operated motor for a running machine.



The code is written to meet the following specification:

- If the start switch is on and the runner is sensed, the motor switches on.
- The motor operates using pulse-width modulation (PWM) with a mark to space ratio of 1:3.
- The sequence repeats.

The pin connection table is shown below.

Input connection	Pin	Output connection
	7	motor
runner sensor (high when sensed)	1	
start switch	0	

Part of the same program is shown below in PBASIC and ARDUINO code.

```
PBASIC
```

main: if pin 0 = 0 then main	
if pin 1 = 1 then main	
pwm: high 7	
pause 15	
low 7	
pause 15	
goto main	

ARDUINO

```
void loop() {
    if (digitalRead(pin0)==LOW){
        loop();}
    if (digitalRead(pin1)==HIGH){
        loop();}
}
void pwm(){
    digitalWrite(pin7,HIGH);
    delay(15);
```

digitalWrite(pin7,LOW);

DO NOT

WRITE IN THIS MARGIN

```
delay(15);
return;
}
```

page 08

X 8 2 3 7 6 0 1 0 8 *


(co)	ntinued)													
Two	faults in the o	code opp	osite are	e show	n in b	old.								
(a)	Correct the two corrected codes of the two corrected codes of the two codes of two		ent fault	s in th	e pro	gram	орр	osite	e by	' wr	itin	g th	ie	
	You may show	w correcti	ons for	either	PBAS	C or <i>i</i>	ARDI	ЛИС).					2
	Correction 1													_
	Correction 2													_
(b)	Complete the 1:3.	e graph be	elow to s	show a	PWN	signa	al wi	th a	ma	ırk t	to sj	bac	e ratio of	_
	You must sho	ow at least	t three p	oulses.										2
	voltage (V)												7	
	-												-	
	-											-	-	
	-											_	-	
													_	
	L			+ + +		+ +	+ +	+ +		-		+ t	time (ms)	
												I	Turn ove	r



SECTION 2 — 90 marks Attempt ALL questions

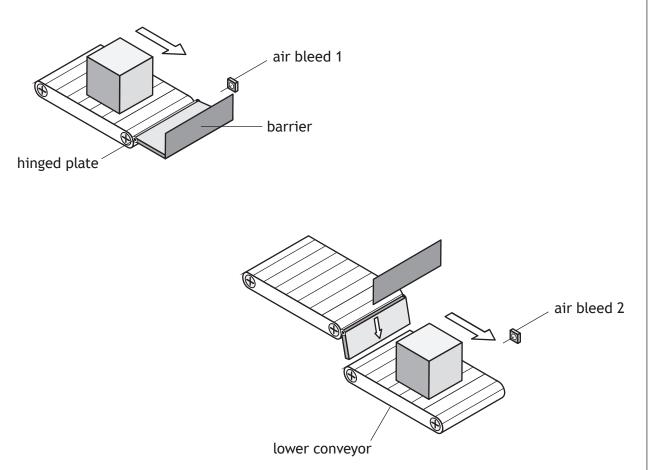7. A packaging process in a factory is to be automated.

When a package reaches the end of a conveyor it is to be held in place while two staples are attached to seal the package closed. It is then released to the next stage of the process.



The full operation of the pneumatic circuit is described below:

- When the package is sensed by an air bleed operated diaphragm (air bleed 1), cylinder A outstrokes to hold the package in place.
- After a controlled delay, cylinders B and C outstroke to close the package lid and staple it in place.
- After a further controlled delay, cylinders A, B, C and D instroke and the package is allowed to drop down to the lower conveyor.
- When the package is sensed by air bleed 2, cylinder D outstrokes to close the chute.



[Turn over for next question


DO NOT WRITE ON THIS PAGE



DO NOT WRITE IN THIS MARGIN

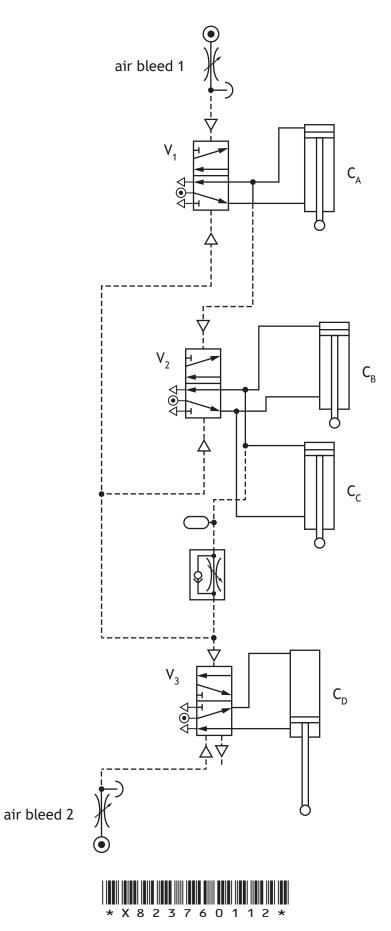7. (continued)

A proposed design for the pneumatic control system is shown below.




7	(MARKS	DO NOT WRITE IN THIS MARGIN
7.		ntinued) Identify three faults with the design shown opposite, and describe how each		
		one should be corrected.	6	
		Fault 1	_	
			_	
			_	
			_	
		Fault 2	_	
			_	
			_	
			_	
			_	
		Fault 3	_	
			_	
			_	
			_	
			_	
		[Turn ove	r	
		* X 8 2 3 7 6 0 1 1 3 *	-	

				MARKS	DO NOT WRITE IN THIS MARGIN			
7.	(cont	inue	d)					
		An engineer considered using electronically-controlled mechanical systems to operate this process instead of pneumatics.						
	(b)	(i)	Describe two environmental reasons why pneumatics was the preferred option.	2				
			Reason 1	_				
				_				
				_				
			Reason 2	_				
				_				
				-				
				-				
		(ii)	Describe how a mechanical engineer applies mathematical skills when designing a pneumatic system.	1				
				_				
				-				
				_				



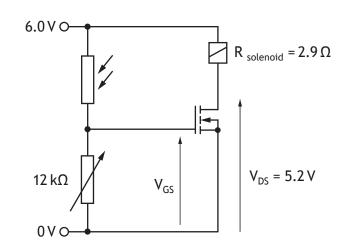7. (continued)

A further part of the control system requires valves to be actuated by electronic signals when a sensor is exposed to light. The control circuit for a solenoid actuator is shown below.



The characteristics of the circuit are shown in the table below.

Gate voltage (V _{GS})	Current (I _{DS})
5.5 V	430 mA
5.0 V	415 mA
4.5 V	362 mA
4.2 V	276 mA
4.0 V	88.3 mA
3.8 V	12.4 mA

(c) Determine, using this table, the gate voltage (V_{GS}) for the conditions in the circuit above.

3

page 15

MARKS DO NOT WRITE IN THIS MARGIN

7. (continued)

The factory also produces frosted glass sheets, and they must be tested before they are packaged.

A system is needed to check that a certain amount of light can pass through these sheets and record how many are suitable for packaging.

A preliminary design must meet the following specification:

- A position sensor detects when a sheet is in position for testing.
- When a sheet is in position, a light source switches on and a reading is taken from an analogue light sensor.
- If the reading from the sensor is between 50 and 100, a pneumatic cylinder outstrokes for one second to push the sheet into a packing area.
- If the reading is less than 50 or more than 100, the sheet is removed by an operator for disposal.
- When the sheet is no longer detected in position the process restarts.
- When 10 sheets meet the requirements, the light source switches off and the system stops.

The table below identifies the connections to the microcontroller.

Input	Pin	Output
	7	pneumatic cylinder control
	6	light source
position sensor	1	
light sensor (analogue)	0	


(d) Complete, with reference to the specification and the input/output table, the flowchart shown opposite for the control of the system.

5



page 16

7. (d) (continued)

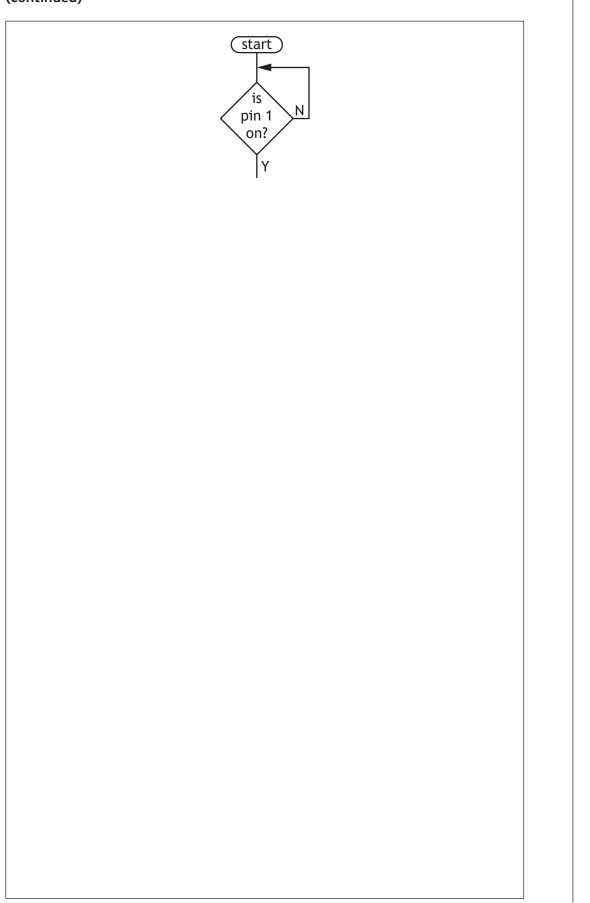



[Turn over

DO NOT WRITE IN THIS MARGIN


page 17

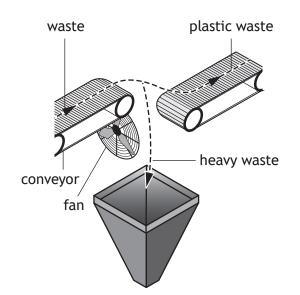8. A recycling plant is developing a system to separate different types of waste so that they can be packed and sold to manufacturers.

DO NOT WRITE IN THIS MARGIN



One stage of the process uses weight sensors to detect plastic waste. Jets of air from a fan are then used to separate the plastic waste from heavier items such as metal waste.





[Turn over for next question

DO NOT WRITE ON THIS PAGE




1

8. (continued)

A circuit to control the action of the fan motor is shown below. The strain gauges have a resistance of 120 Ω unless they are stretched or compressed.

Strain gauge A is used as an active strain gauge to detect the weight of the waste. Strain gauge B is used as a passive strain gauge.

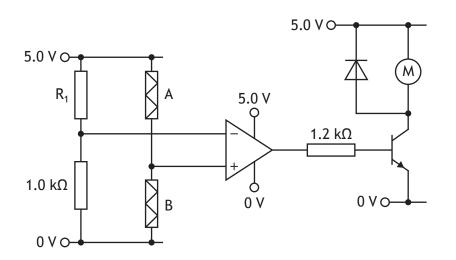When strain gauge A has a resistance of 119 Ω the fan motor must switch on.




(a) Calculate the value of R_1 .

(b) Describe the purpose of strain gauge B in this situation.



page 20

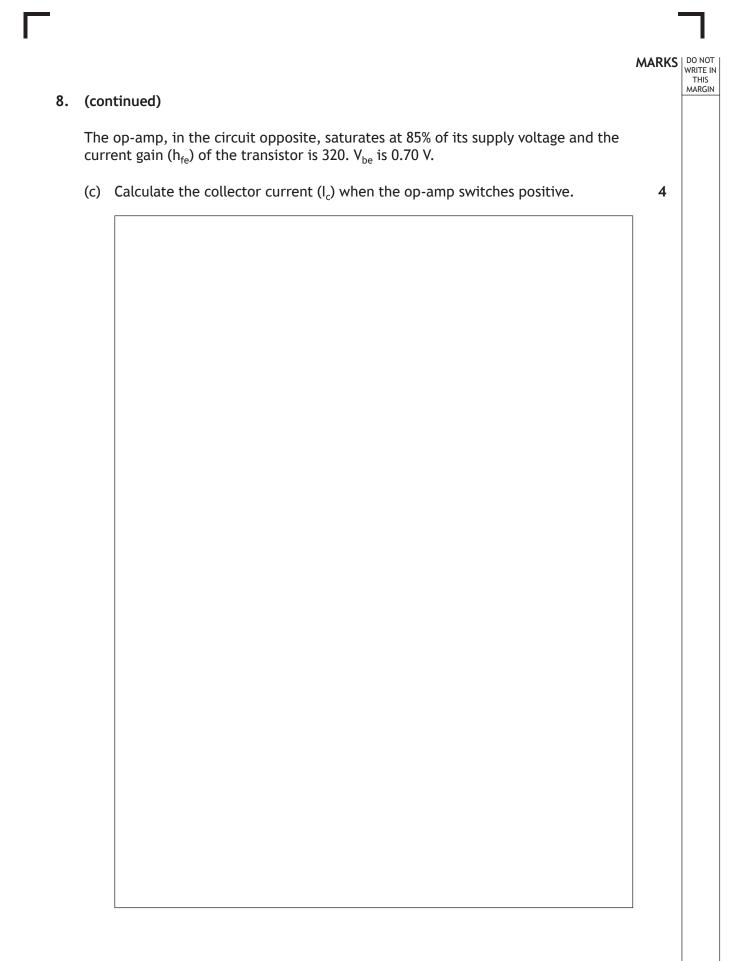


[Turn over




(continued) 8.

After testing, it is decided that the fan motor should only operate if the weight sensed is between two set levels.

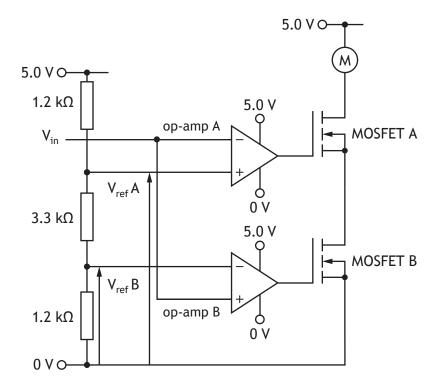The circuit used to perform this operation is shown below.



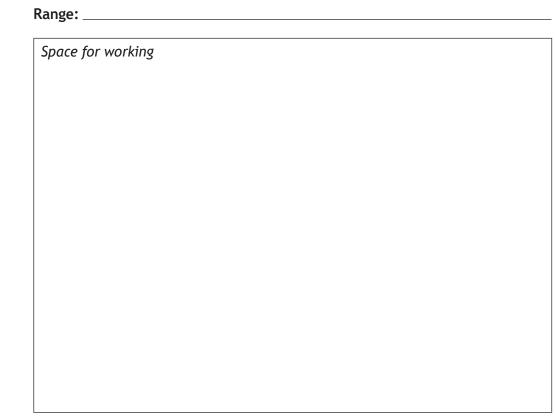(d) Determine the range of values of $V_{\rm in}$ that will cause the motor to turn.





MARKS DO NOT WRITE IN THIS MARGIN


-	,		MARKS	DO NOT WRITE IN THIS MARGIN
8.	(cor	ntinued)		
	(e)	Describe, with reference to all the components, how the circuit shown opposite operates as V_{in} increases from 0 V to 5.0 V.	3	
		When V _{in} is at 0 V	-	
			-	
			-	
			-	
			-	
			-	
			-	
			-	
			-	
			-	
			-	
		[Turn over	-	
				I




MARKS DO NOT WRITE IN THIS MARGIN

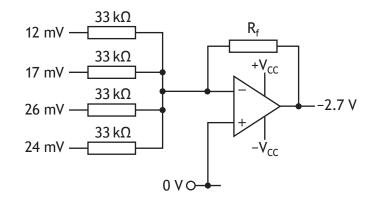8. (continued)

When materials have been separated, they are collected into bales and are weighed. Four sensors are used to ensure an accurate reading is achieved.



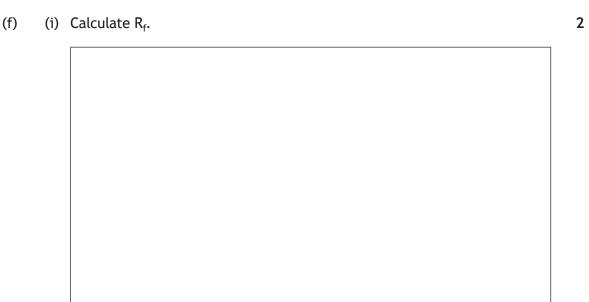The test circuit above combines the outputs of the four sensors into one signal.






8. (f) (continued)

The output voltage from the circuit is required to be positive.

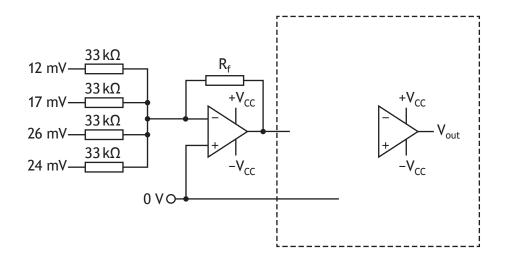(ii) Complete the circuit diagram below, to show how the output voltage could be converted to a positive value of the same magnitude. Include resistor values on your diagram.



[Turn over



MARKS WRITE IN THIS MARGIN


9. A range of street sweepers are being developed to clean outdoor areas.

MARKS DO NOT WRITE IN THIS MARGIN

4




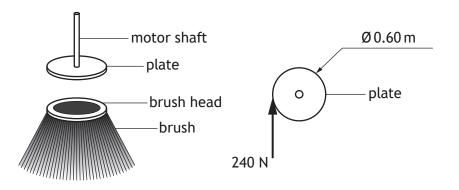The street sweeper makes use of various rotating brushes which collect dirt and debris. Each brush is connected to a plate which is driven by a motor shaft as shown below.



The diameter of the plate is 0.60 m and the force exerted onto the plate when the brush is in motion is 240 N. The motor is rated at 220 V, 6.6 A. Assume the system is 100% efficient.

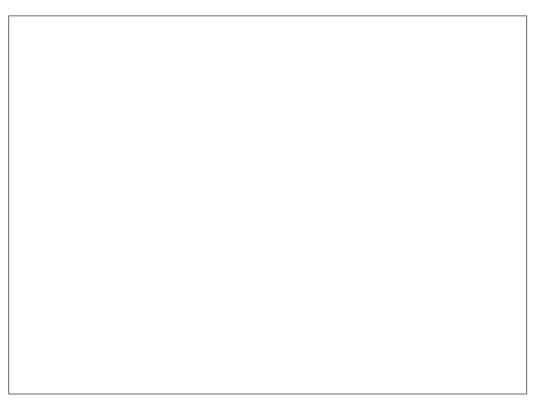(a) Calculate the rotational speed of the motor.






9. (continued)

During assembly, the plate and brush head were secured using three steel bolts. The ultimate tensile stress of the steel is 430 Nmm^{-2} .

Each bolt is initially tightened to a stress of 5.5 Nmm⁻². A load of 5.0 kN is then applied to each bolt adding further stress.

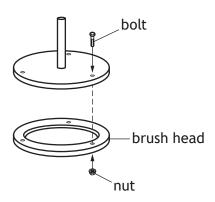A factor of safety of 3.0 is applied to each bolt.



(b) Calculate the required diameter of each bolt.

4

MARKS DO NOT WRITE IN THIS MARGIN


[Turn over



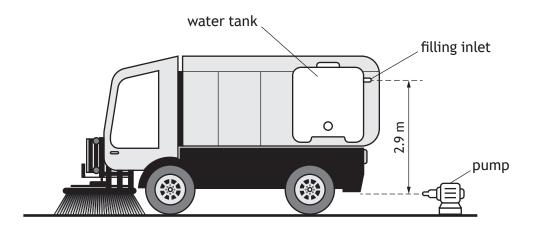9. (continued)

Water from a tank is sprayed during the cleaning process. The tank holds 2500 litres of water.

```
Note: 1.0 litre of water = 1.0 kg
```



The water tank is filled using an electrical pump, rated at 230 V and 5.0 A. The pump is 87% efficient and the filling inlet is located 2.9 m above the pump.

(c) Calculate the time it will take to fill an empty tank.



MARKS DO NOT WRITE IN THIS MARGIN (continued) 9. Member A is a structural member used to support and secure the empty water tank at the rear of the street sweeper. Ø 37 mm member A Ο Member A is a tube with an inner diameter of 37 mm. The force from the empty water tank acting vertically on the member is 625 N and the stress present is 3.4 Nmm⁻². (d) Calculate the wall thickness of member A. 5




10. A biomass plant converts waste food and other organic material into useful energy.

DO NOT WRITE IN THIS MARGIN




The waste is stored and allowed to decompose producing heat and useful gas. If it gets too hot it presents a fire hazard, so a warning system is required.

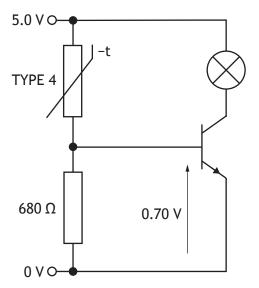A circuit, designed to give a visual warning when the temperature is too high, is shown below.





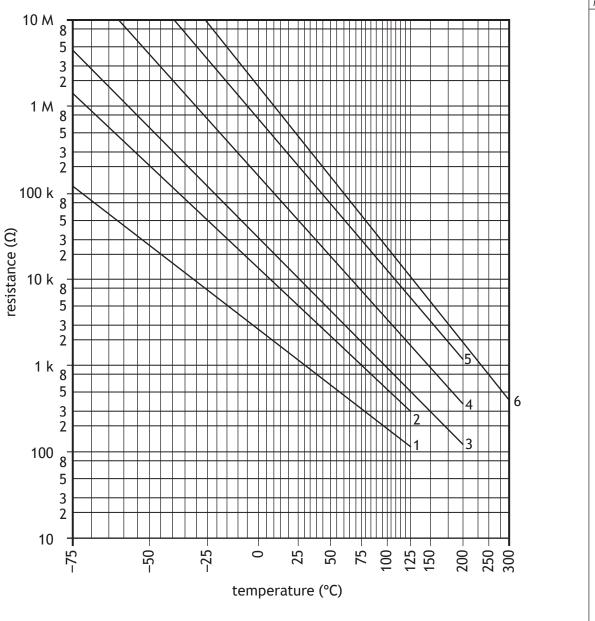

(i) Calculate the current through the thermistor when the temperature (a) reaches 120 °C and the visual warning is on.



MARKS DO NOT WRITE IN THIS MARGIN

10. (a) (continued)

(ii) Calculate the base current.

The useful gas produced by the biomass plant is stored in canisters. An automated system is used to fit a cap onto a canister once it has been filled.

MARKS DO NOT WRITE IN THIS MARGIN

2

2


The movement of a motor involved in the process of securing the cap in place needs to be maintained at a steady speed.

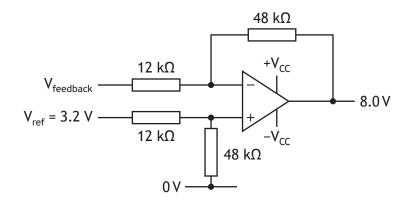(b) Explain why a two-state control system may **not** be suitable for this situation.



(continued) 10.

A proportional control system is chosen for the final design to control the speed of the motor. The circuit for part of the control system is shown.



(c) Calculate the voltage from the feedback sensor.

[Turn over



page 33

MARKS DO NOT WRITE IN THIS MARGIN

MARKS DO NOT WRITE IN THIS MARGIN (continued) 10. The graph shows how the speed of the motor initially changes when the proportional control system is switched on. speed desired speed · ----time (d) Describe how the speed of the motor would change if the gain of the op-amp was increased. Include the initial response to this change and the speed of the motor over time. You may use the graph above to illustrate your answer. 3

* X 8 2 3 7 6 0 1 3 4 *

[Turn over for next question


DO NOT WRITE ON THIS PAGE




10. (continued)

Once filled, the canisters are placed in a crate to be lifted to a storage facility. Part of the lifting assembly is shown below.

DO NOT WRITE IN THIS MARGIN

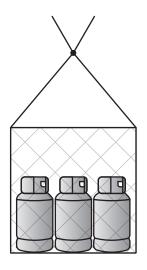


The forces acting on part of the lifting assembly are shown below.

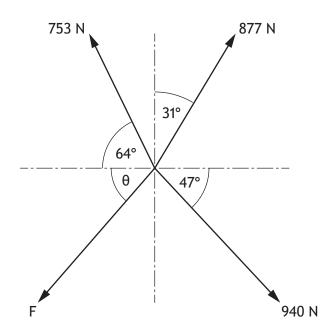




page 36

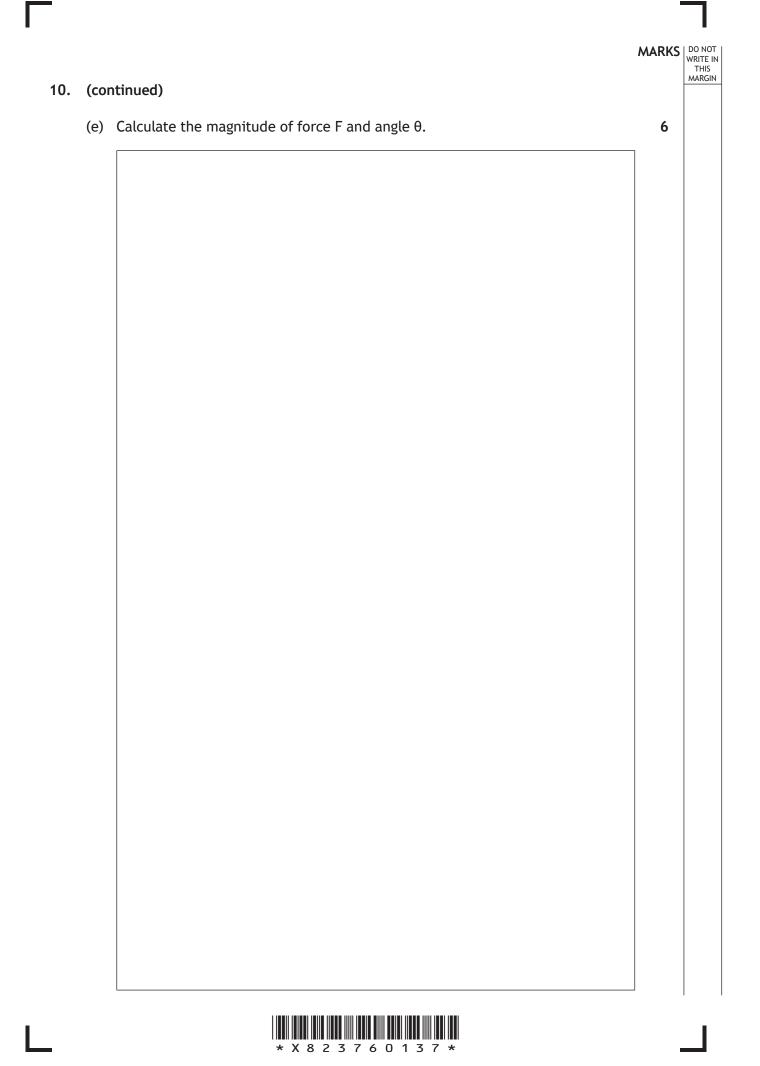

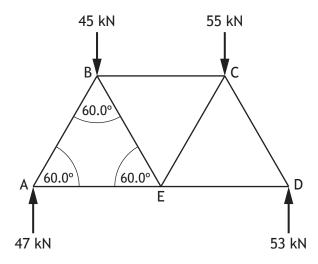11. As a commitment to increasing the use of electric public transport, a city is developing a railway and traffic management system.



A proposed structural design for a frame to support part of the railway is shown below. The frame is based on equilateral triangles.



(a) Calculate, using nodal analysis, the magnitude and nature of the forces inside members AB, AE, BE and BC.

Show all working and final units on the page opposite.


Complete the table below.

Member	AB	AE	BE	BC
Force				
Nature	strut	tie		



6

11. (a) (continued)

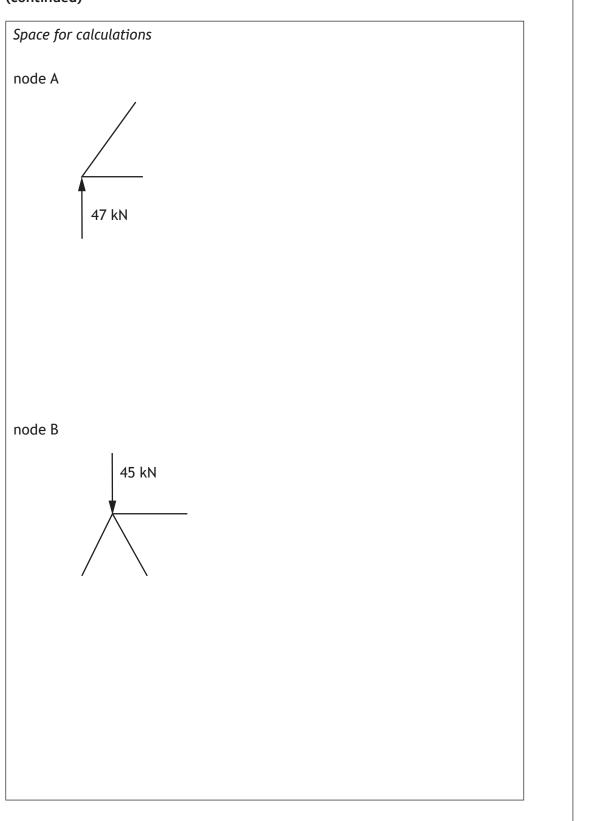

[Turn over


DO NOT WRITE IN THIS MARGIN



4

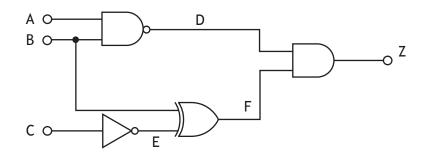11. (continued)

An initial design for a control system to operate the doors on a train to be used on the railway is shown.



(b) (i) Complete the truth table for the logic diagram.Include the intermediate logic values for D, E, and F and the output Z.

Α	В	С	D	E	F	Z
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				



MARKS DO NOT WRITE IN THIS MARGIN 11. (b) (continued) The design for a control system which operates part of the traffic management system is shown below. A O-B O--0 Z C O-(ii) Complete a Boolean equation to describe the operation of this circuit. 3 Z = _____ (iii) Draw a NAND equivalent for this circuit. Simplify where appropriate. 4



		MARKS	DO NOT WRITE IN THIS	
(coi	ntinued)		MARGIN	
The design phase of the traffic management system was carried out by an electronic engineer.				
(c)	Describe how two pieces of specialised knowledge would be used by an electronic engineer during the design phase of the traffic management system.			
	Knowledge 1	-		
		-		
		-		
		-		
(d)	Describe two ways these improvements would have a positive social impact on those who live in, work in, or visit the city.	2		
	Impact 1	-		
		-		
		-		
	Impact 2	-		
		-		
		-		
	[END OF QUESTION PAPER]			
	The elec (c) Tea thro	electronic engineer. (c) Describe how two pieces of specialised knowledge would be used by an electronic engineer during the design phase of the traffic management system. Knowledge 1	(continued) The design phase of the traffic management system was carried out by an electronic engineer. 2 (c) Describe how two pieces of specialised knowledge would be used by an electronic engineer during the design phase of the traffic management system. 2 Knowledge 1	



MARKS DO NOT WRITE IN THIS MARGIN

ADDITIONAL SPACE FOR ANSWERS



ADDITIONAL SPACE FOR ANSWERS



L

DO NOT WRITE ON THIS PAGE



DO NOT WRITE ON THIS PAGE



L

DO NOT WRITE ON THIS PAGE



DO NOT WRITE ON THIS PAGE

Acknowledgement of copyright

- Question 1 Daniel Jedzura/shutterstock.com
- Question 2 SB_photos/shutterstock.com
- Question 4 chuyuss/shutterstock.com
- Question 6 Value ho/shutterstock.com
- Question 8 Nordroden/shutterstock.com
- Question 9 Mike_shots/shutterstock.com
- Question 10 Kletr/shutterstock.com
- Question 11 Sergio Photone/shutterstock.com

